

Course BE(EEE(M))

Batch 14

Semester VII

Subject Code EE1701

Subject Name Solid State Drives

Unit-I Drive Characteristics

PART-A

- 1 What is meant by electrical drives?
- 2 Draw the electric drive system.
- 3 Specify the functions of power modulator.
- 4 Mention the different types of drives.
- 5 Define Passive torque.
- 6 What are the advantages of electric drives?
- 7 what are the functions performed by electric drives?

- 8 What are the disadvantages of electric drives?
- 9 What are the advantages of group drive over individual drive?
- 10 Define Active torque.
- 11 Mention the types of braking.
- 12 List the parts of electrical drives.
- 13 Mention the applications of electrical drives.
- 14 Mention the different types of classes of duty.
- 15 What is meant by regenerative braking?
- 16 What is meant by dynamic braking?
- 17 What is meant by plugging?
- 18 What is critical speed?
- 19 Which braking is suitable for reversing the motor?
- 20 What are the methods of operation of electric drives?

Part-B

- 1 Mention the different factors for the selection of electric drives?
- 2 Why the group drive is not used extensively?
- 3 Explain about electric drives classification.
- 4 Write short notes on types of electric drives.
- 5 Explain about the components of load torques.
- 6 Difference between AC and DC drives.
- 7 Explain about the dynamics of motor load system in detail.

PART-C

- 1 Draw and explain the Characteristics of Different types of Loads.
- 2 Explain in detail about Multi quadrant Operation with neat sketch.
- 3 Explain in detail about Steady State Stability.
- 4 Explain in detail about regenerative braking.

- 5 Explain in detail about General electric drive system.

UNIT- II CONVERTER / CHOPPER FED CHARACTERISTICS

PART-A

- 1 Which braking is suitable for reversing the motor?
- 2 What is meant by mechanical characteristics?
- 3 What are the advantage and disadvantages of D.C. drives?
- 4 What is the use of flywheel? Where it is used?
- 5 Why the variable speed applications are dominated by D.C. drives?
- 6 What are the advantages of series motor?
- 7 How the D.C. motor is affected at the time of starting?
- 8 Define and mention different types of braking in a dc motor?
- 9 List the drawbacks of armature resistance control?

- 10 Mention the methods of armature voltage controlled dc motor?
- 11 Mention the drawbacks of rectifier fed dc drives?
- 12 Write the expression for average o/p voltage of full converter fed dc drives?
- 13 What are the advantages in operating choppers at high frequency?
- 14 State the advantages of dc chopper drives?
- 15 What is chopper?
- 16 What is duty cycle?
- 17 What is constant frequency system?
- 18 What is variable frequency system?
- 19 What is time ratio control?
- 20 What is Current limit Control?

PART-B

- 1 Explain the operation of a two quadrant chopper fed DC drives.
- 2 Explain the operation of a one quadrant chopper fed DC drives.

- 3 Explain the two different types of speed control of D.C Motor.
- 4 Explain any two different types of braking in a dc motor.
- 5 Explain the different types of control techniques of chopper in detail.
- 6 Explain in detail about rheostatic braking in dc motor.
- 7 Describe with a neat diagram the operation of four quadrant converter.
- 8 Discuss the two methods of time ratio control.
- 9 Explain using a power circuit the working of a single phase semi converter fed separately excited motor drive.

Part-C

- 1 Describe the operation of single phase fully controlled rectifier control of separately excited DC motor with neat waveforms.
- 2 Explain in detail about CLC and TRC methods with diagram.
- 3 Explain the operation of four quadrant DC chopper.

- 4 Explain about the Ward —Leonard method of speed control of DC motor.
- 5 Describe the operation of three phase fully controlled rectifier control of separately excited DC motor with neat waveforms.

Unit-III INDUCTION MOTOR DRIVES

PART-A

- 1 what are the types of induction motor?
- 2 What is indirect flux control?
- 3 What is voltage source inverter?
- 4 What is the purpose of inductance and capacitance in the D.C. link circuit?
- 5 Define Harmonics.
- 6 What is slip controlled drive?
- 7 What are the effects of harmonics ?
- 8 What is a current source inverter?

- 9 Explain about the commutation of the current source inverter.
- 10 Give the features from which a slip controlled drive is developed.
- 11 Difference between VSI and CSI fed drive.
- 12 What are the advantages and disadvantages of rotor resistance control?
- 13 Where is rotor resistance control used?
- 14 What are the disadvantages of rotor resistance control?
- 15 How is the resistance in the output terminals of a chopper varied?
- 16 What is the function of inductance L and resistance R in the chopper resistance circuit?
- 17 What are the disadvantages and advantages of chopper controlled resistance in the rotor circuit method?
- 18 How is the range of speed control increased?
- 19 " Why the static scherbius drive has a poor power factor?"

PART-B

- 1 Draw and explain the torque-speed characteristics of induction motor.
- 2 Explain about Stator voltage control in detail.
- 3 Explain about stator frequency control in detail.
- 4 List the advantages and disadvantages of stator voltage control.
- 5 List the effects of low frequency and high frequency induction motor drive.
- 6 Explain in detail about closed loop v/f induction motor drive.
- 7 Explain in detail about VSI fed induction motor drive.
- 8 Explain in detail about constant air gap flux control induction motor drive.
- 9 Explain about Rotor resistance control of induction motor drive.
- 10 List the advantages and disadvantages of rotor resistance control.
- 11 Explain in detail about closed loop of static rotor resistance control.
- 12 Explain in detail about closed loop of static Kramer system.
- 13 Explain in detail about closed loop of static scherbius system.

14 Explain in detail about CSI fed induction motor drive.

Part-C

- 1 Explain the operation of constant air gap flux control.
- 2 Explain the operation of constant slip speed control.
- 3 Explain the induction motor operation when the V / f ratio is held constant .
- 4 Draw and explain the slip power recovery scheme applicable for three phase slip- ring induction motor.
- 5 Using a diagram and speed- torque curve, explain the stator voltage control scheme for the speed control of a three phase induction motor.

Unit-IV SYNCHRONOUS MOTOR DRIVES

PART-A

- 1 Give the four modes of operation of a Scherbius drive

- 2 " Give the use of synchronous motors."
- 3 How are the stator and rotor of the synchronous motor supplied?
- 4 What is the difference between an induction motor and synchronous motor?
- 5 List out the commonly used synchronous motors.
- 6 Mention the main difference between the wound field and permanent magnet motors.
- 7 what is the relation between frequency and inductive reactance ?What happens if frequency increases?
- 8 List the advantages of stator voltage control.
- 9 Mention the two modes employed in variable frequency control.
- 10 How power factor is improved by synchronous motor drive?
- 11 What are the two types of static scherbius system?
- 12 List the effects of low frequency control induction motor drive.
- 13 List the control strategies of Voltage/frequency control.
- 14 List the effects of high frequency control induction motor drive.

- 15 What are the disadvantages of VSI fed synchronous motor drive?
- 16 List the disadvantages of stator voltage control.
- 17 Define Slip.
- 18 What are the disadvantages of cycloconverter?
- 19 What are the applications of cycloconverter?
- 20 Give the application of CSI fed synchronous motor.

Part-B

- 1 Explain in detail about v/f permanent magnet synchronous motor.
- 2 Explain in detail about open loop volts/Hertz synchronous motor drive.
- 3 Explain about self control of Synchronous motor drive.
- 4 Explain about field oriented control of Permanent magnet synchronous motor.
- 5 Explain about constant torque control of synchronous motor.
- 6 Explain in detail about flux weakening control of PM Synchronous motor drive.

- 7 Explain in detail about PMSM Drive with Active Power Factor Correction.
- 8 Explain in detail about Closed loop control PMSM drive.
- 9 Explain about of power factor correction circuit with boost converter.
- 10 Explain about VSI fed synchronous motor drive.
- 11 Explain about HYSTERESIS Current Controller.
- 12 Explain about Power factor improvement of synchronous motor.
- 13 Explain about Constant torque and flux weakening of synchronous motor drive.

PART-C

- 1 Explain with the block diagram of marginal angle control of synchronous motor drive.
- 2 Explain Power factor control of synchronous drive.
- 3 Describe the self control of synchronous motor.

- 4 Explain the closed loop control system of adjustable speed synchronous motor drives.
- 5 Explain the construction and operation of permanent magnet synchronous motor.
- 6 Explain in detail about the brushless DC motor drive.

Unit-V DESIGN OF CONTROLLERS FOR DRIVES

PART-A

- 1 What is meant by frequency control of IM?
- 2 What is meant by V/F control?
- 3 What are the advantages of V/F control?
- 4 What is meant by stator current control?
- 5 What are the 3 modes of region in the adjustable-freq IM drives characteristics?
- 6 What are the two modes of operation in the motor?
- 7 How will you select the motor rating for a specific application?

- 8 What is braking? Mention its types.
- 9 What are the three types of speed control?
- 10 What are the advantages of armature voltage control?
- 11 What are the methods involved in armature voltage control? When the supply is A.C.
- 12 Give some drawbacks and uses of Ward-Leonard drive.
- 13 Give some advantages of Ward-Leonard drive.
- 14 What is the use of controlled rectifiers?
- 15 What is known as half-controlled rectifier and fully controlled rectifier?
- 16 What is called continuous and discontinuous conduction?
- 17 What are the three intervals present in discontinuous conduction mode of single phase half and fully controlled rectifier?
- 18 What is called inversion?
- 19 What are the limitations of series motor? Why series motor is not used in traction applications now days?

20 What are the advantages of induction motors over D.C. motors?

PART-B

- 1 Derive the armature control of dc motor drive.
- 2 Explain about closed loop speed control of dc motor.
- 3 Explain about inner current loop control of dc motor.
- 4 Explain about Speed control by armature voltage variation.
- 5 Explain about speed control by flux weakening method.
- 6 Explain the block diagram of speed controller of dc machine.
- 7 Explain about block diagram of current controller of dc machine.
- 8 Explain any two methods of speed control of dc machine.
- 9 Explain about different speed control of shunt motor.
- 10 Explain about different speed control of series motor.
- 11 Explain about speed control of constant speed motor.
- 12 Explain about speed control of constant torque motor.

13 Explain about armature voltage control of dc motor drive.

14 Explain about field control of dc motor drive.

PART-C

1 Derive the transfer function of separately excited DC motor and load.

2 Explain in detail about design of speed controller and current controller for dc drives.

3 Describe the closed loop speed control of separately excited DC motor by proportional controller.

4 Explain the current limit control of separately excited DC motor.

5 Write short notes on : (i) Field weakening mode control, (ii) Armature voltage control .

6 Explain in detail about converter selection and characteristics.